



Lab 4: Frequency Domain Circuits

Key Concepts:

- ❖ Decibels (dB)
- ❖ Steady-state signals; Fourier series
- ❖ Complex impedances
- ❖ Low-pass and high-pass filters
- ❖ Frequency response
- ❖ Time domain vs. frequency domain
- ❖ Fourier transform, Fast Fourier Transform (FFT)



Decibels

$$\text{Ratio} = P_2/P_1 \quad (\text{linear})$$

$$\text{Ratio (dB)} = 10 \log_{10}(P_2/P_1) \quad (\text{dB})$$


$$P_{\text{out}} = 10 P_{\text{in}} \Rightarrow \text{Gain} = 10 \log_{10}\left(\frac{10 P_{\text{in}}}{P_{\text{in}}}\right) = 10 \text{ dB}$$

$$P_{\text{out}} = 0.1 P_{\text{in}} \Rightarrow \text{Gain} = 10 \log_{10}\left(\frac{0.1 P_{\text{in}}}{P_{\text{in}}}\right) = -10 \text{ dB}$$

$$P_{\text{out}} = P_{\text{in}} = 10 \log_{10}(1) = 0 \text{ dB}$$

$$P_{\text{out}} = 0.5 P_{\text{in}} \Rightarrow = 10 \log_{10}(0.5) = -3 \text{ dB}$$
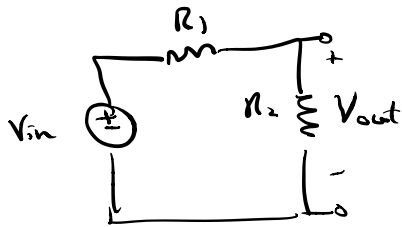
$$\log x^n = n \log x$$
$$\log x^2 = 2 \log x$$



$$P = V^2/R$$

$$P_{\text{out}} = V_{\text{out}}^2/R$$

$$P_{\text{in}} = V_{\text{in}}^2/R$$

$$\Rightarrow 10 \log_{10}\left(\frac{V_{\text{out}}^2/R}{V_{\text{in}}^2/R}\right) = 10 \log_{10}\left(\frac{V_{\text{out}}^2}{V_{\text{in}}^2}\right)$$
$$= 20 \log_{10}\left(\frac{V_{\text{out}}}{V_{\text{in}}}\right)$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} \quad (\text{dB})?$$

Decibels cont.

$$\frac{P_{\max}}{P_{\min}} = \text{Dynamic Range (linear)}$$

$$10 \log_{10} \left(\frac{P_{\max}}{P_{\min}} \right) = \text{DR (dB)}$$

$$20 \log_{10} \left(\frac{V_{\max}}{V_{\min}} = \frac{10 \text{ V}}{0.1 \text{ mV}} \right) = 100 \text{ dB} \rightarrow 5 \text{ orders of magnitude}$$

$$\text{dBW} : \text{ decibels relative to 1W} : 10 \log_{10} \frac{P_1 \rightarrow 100\text{W}}{1\text{W}} = 20 \text{ dBW}$$

$$\text{dBV} : \text{ dB relative to 1V} : 20 \log_{10} \left(\frac{V_1 \rightarrow 10\text{V}}{1\text{V}} \right) = 20 \text{ dBV}$$



dBV_{rms}

$$\text{dBm} : \text{ dB relative to 1 mW} : \begin{matrix} P = 1\text{W} \\ = 10 \log_{10} \frac{1\text{W}}{1\text{mW}} = 30 \text{ dBm} \end{matrix}$$

Steady-state signals

- AC source ; circuit is turned on, allowed to "settle" to "steady state"
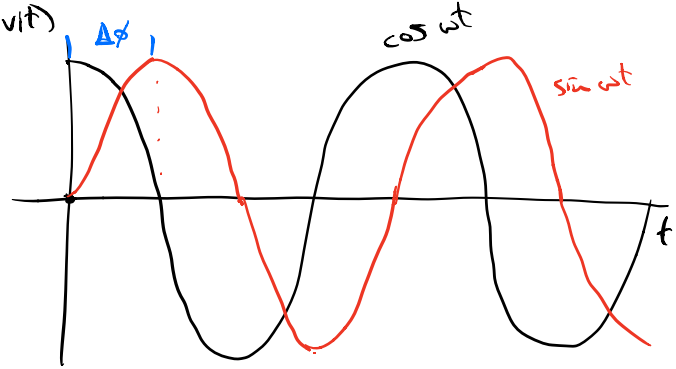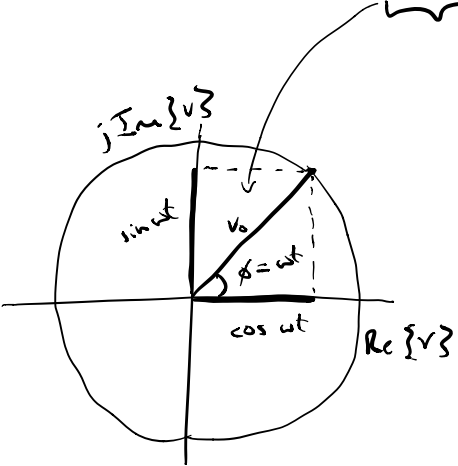
$$\text{signal} = v(t) = V_0 e^{j\omega t} = V_0 (\cos \omega t + j \sin \omega t) \quad \checkmark$$



Fourier Series



Any periodic signal can be decomposed into a sum of sinusoids

$$v(t) = a_0 + \sum_{i=1}^{\infty} (a_i \cos \omega_i t + b_i \sin \omega_i t) = a_0 + \sum_{i=1}^{\infty} c_i e^{(j\omega_i t + \phi_i)}$$

a_0 = DC component
offset

ω_i = frequencies = $i \frac{2\pi}{T}$

$v(t) \rightarrow a_0, a_i, b_i$

$$a_0 = \frac{1}{T} \int_0^T v(t) dt$$

$$a_i = \frac{2}{T} \int_0^T v(t) \cos \omega_i t dt$$


$$c_i = \sqrt{a_i^2 + b_i^2}$$

$$\phi_i = -\tan^{-1} \left(\frac{b_i}{a_i} \right)$$

$$b_i = \frac{2}{T} \int_0^T v(t) \sin \omega_i t dt$$

Fourier Series Example 1
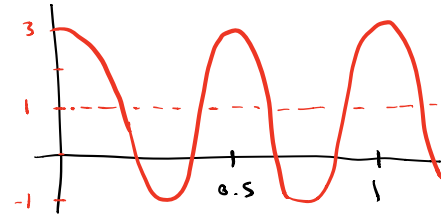
$$v(t) = 1 + 2 \cos(4\pi t) \quad \checkmark$$
$$=$$
$$\omega = 4\pi$$
$$T = \frac{2\pi}{\omega} = \frac{2\pi}{4\pi} = 0.5$$



$$a_0 = \frac{1}{T} \int_0^T v(t) dt = 1$$
$$\omega_i = i \frac{2\pi}{T}$$

$$a_i = \frac{2}{T} \int_0^T (1 + 2 \cos 4\pi t) (\cos \omega_i t) dt$$


$$a_1 = \frac{2}{T} \int_0^T (1 + 2 \cos 4\pi t) \cos 4\pi t dt = 2$$

$$b_1 = \frac{2}{T} \int_0^T (1 + 2 \cos 4\pi t) \sin 4\pi t dt = 0$$

$$a_2, b_2, a_3, b_3, \dots = 0$$



$$v(t) = a_0 + \sum_{i=1}^{\infty} (a_i \cos \omega_i t + b_i \sin \omega_i t)$$
$$= \frac{1 + 2 \cos 4\pi t}{1} + 0 \sin 4\pi t$$
$$+ 0 \cos 8\pi t + 0 \sin 8\pi t \dots$$

Example 2: Square wave


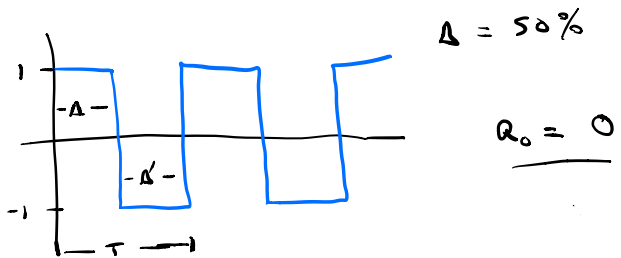


$$a_1 = \frac{2}{T} \int_0^T v(t) \cos\left(\frac{2\pi}{T}t\right) dt$$
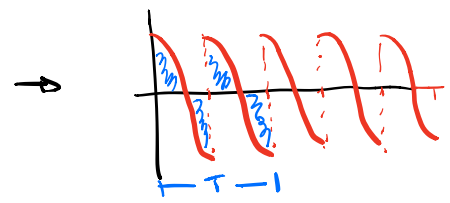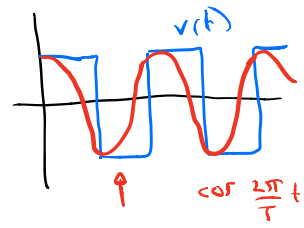
$$= 0 \quad \underline{a_i = 0 \text{ for all } i}$$


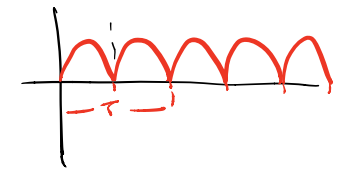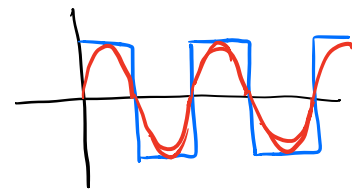
$$b_1 = \frac{2}{T} \int_0^T v(t) \sin\left(\frac{2\pi}{T}t\right) dt$$




$$b_1 = \frac{2}{T} \left[2 \int_0^{T/2} \sin\left(\frac{2\pi}{T}t\right) dt \right] = \frac{4}{\pi}$$

$$\underline{b_i = 0 \text{ for all even } i}$$

Square Wave cont.

General solution
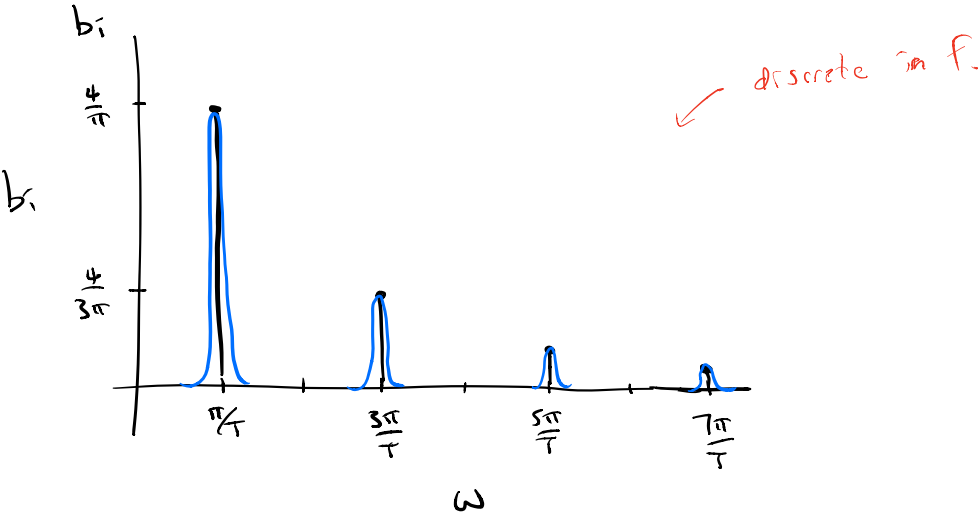
$$v(t) = \frac{4}{\pi} \sum_{s=1,3,5,\dots}^{\infty} \frac{1}{s} \sin\left(\frac{is\pi t}{T}\right)$$



- Algebra
- Applied Mathematics
- Calculus and Analysis
- Discrete Mathematics
- Foundations of Mathematics
- Geometry
- History and Terminology
- Number Theory
- Probability and Statistics
- Recreational Mathematics
- Topology
- Alphabetical Index
- Interactive Entries
- Random Entry
- New in MathWorld
- MathWorld Classroom
- About MathWorld
- Contribute to MathWorld
- Send a Message to the Team
- MathWorld Book

Wolfram Web Resources

13,612 entries
Last updated: Wed Feb 8 2017


*Created, developed, and
nurtured by Eric Weisstein
at Wolfram Research*

- ❖ Square wave is sum of odd harmonics
- ❖ More harmonics included - closer to the truth!

Calculus and Analysis > Series > Fourier Series >

Fourier Series--Square Wave

DOWNLOAD
Wolfram Notebook

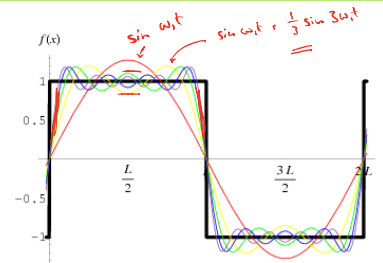

Consider a square wave $f(x)$ of length $2L$. Over the range $[0, 2L]$, this can be written as

$$f(x) = 2[H(x/L) - H(x/L - 1)] - 1, \tag{1}$$

where $H(x)$ is the Heaviside step function. Since $f(x) = f(2L - x)$, the function is odd, so $a_0 = a_n = 0$, and

$$b_n = \frac{1}{L} \int_0^{2L} f(x) \sin\left(\frac{n\pi x}{L}\right) dx \tag{2}$$

reduces to

$$b_n = \frac{2}{L} \int_0^L f(x) \sin\left(\frac{n\pi x}{L}\right) dx \tag{3}$$

$$= \frac{4}{n\pi} \sin^2\left(\frac{1}{2}n\pi\right) \tag{4}$$

$$= \frac{2}{n\pi} [1 - (-1)^n] \tag{5}$$

$$= \frac{4}{n\pi} \begin{cases} 0 & n \text{ even} \\ 1 & n \text{ odd.} \end{cases} \tag{6}$$


The Fourier series is therefore

$$f(x) = \frac{4}{\pi} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \sin\left(\frac{n\pi x}{L}\right). \tag{7}$$

- ❖ Fourier transform is sort-of the continuous (in frequency!) version of Fourier series; rather than sum, it uses integral
- ❖ Operates on any function (Fourier series only works for periodic functions)
- ❖ Fourier transform gives spectrum - separates signal into all of its component frequencies!
- ❖ Determined the magnitude and phase of each component (i.e., each frequency, from $f = -\infty$ to ∞)

$$F(\omega) = \int_{-\infty}^{\infty} f(t)e^{-i\omega t} dt$$
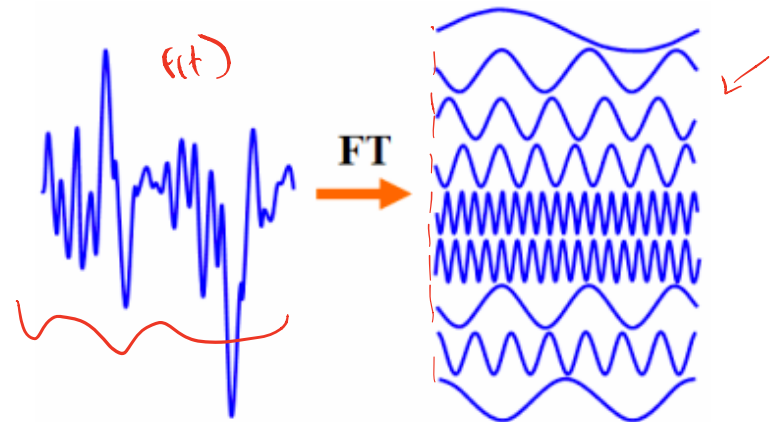
$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(\omega)e^{i\omega t} d\omega$$




Fourier transform of any signal $x(t)$ is given by


$$X(\omega) = \int_{-\infty}^{\infty} x(t) e^{-j\omega t} dt \quad \text{if } x(t) \text{ is in volts, } X(\omega) \text{ is in units of } V \cdot s \text{ or } V/Hz$$

$$\text{inverse FT: } x(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} X(\omega) e^{+j\omega t} d\omega$$

example 1: $x(t) = \delta(t)$

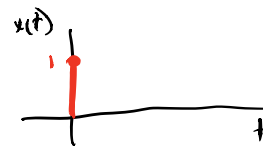
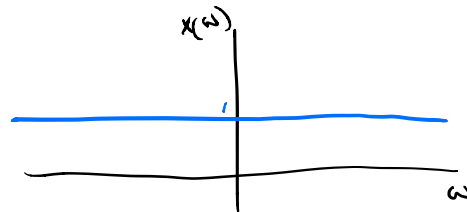
$$X(\omega) = \int_{-\infty}^{\infty} \delta(t) e^{-j\omega t} dt = 1 \quad \text{because } \delta(t) = \begin{cases} 1, & t=0 \\ 0, & \text{elsewhere} \end{cases}$$



More examples


example 2: $x(t) = 1$

$$X(\omega) = \int_{-\infty}^{\infty} 1 \cdot e^{-j\omega t} dt = \delta(\omega), \text{ because } \int_{-\infty}^{\infty} e^{-j\omega t} dt = \begin{cases} 1, & \omega = 0 \\ 0, & \text{elsewhere} \end{cases}$$

$\delta(t) \Leftrightarrow 1$ form a fourier transform pair.

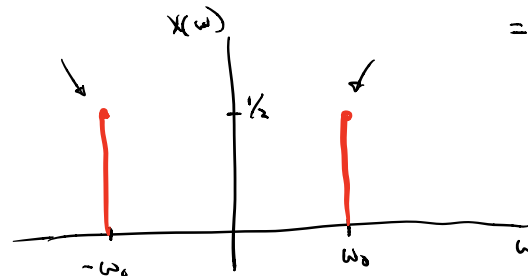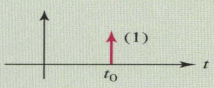
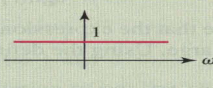
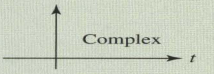
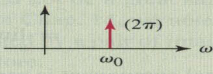
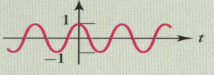
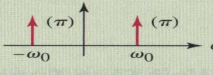

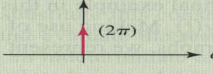
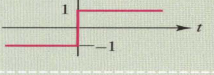
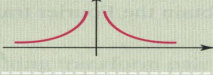
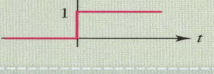
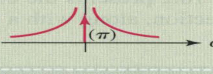
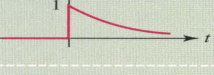
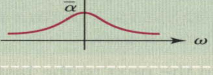
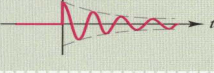
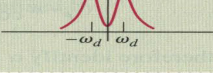
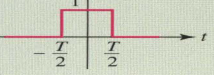
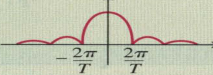
example 3: $x(t) = \cos \omega_0 t$

$$\begin{aligned} X(\omega) &= \int_{-\infty}^{\infty} \cos \omega_0 t e^{-j\omega t} dt \\ &= \int_{-\infty}^{\infty} \left(\frac{e^{j\omega_0 t} + e^{-j\omega_0 t}}{2} \right) e^{-j\omega t} dt = \frac{1}{2} \int_{-\infty}^{\infty} (e^{j(\omega_0 - \omega)t} + e^{-j(\omega_0 + \omega)t}) dt \\ &= \frac{1}{2} (\delta(\omega_0 - \omega) + \delta(\omega_0 + \omega)) \end{aligned}$$



Fourier transform pairs

TABLE 18.2 A Summary of Some Fourier Transform Pairs

$f(t)$	$f(t)$	$\mathcal{F}\{f(t)\} = F(j\omega)$	$ F(j\omega) $
	$\delta(t - t_0)$	$e^{-j\omega t_0}$	
	$e^{j\omega_0 t}$	$2\pi \delta(\omega - \omega_0)$	
	$\cos \omega_0 t$	$\pi [\delta(\omega + \omega_0) + \delta(\omega - \omega_0)]$	
	1	$2\pi \delta(\omega)$	
	$\text{sgn}(t)$	$\frac{2}{j\omega}$	
	$u(t)$	$\pi \delta(\omega) + \frac{1}{j\omega}$	
	$e^{-\alpha t} u(t)$	$\frac{1}{\alpha + j\omega}$	
	$[e^{-\alpha t} \cos \omega_d t] u(t)$	$\frac{\alpha + j\omega}{(\alpha + j\omega)^2 + \omega_d^2}$	
	$u(t + \frac{1}{2}T) - u(t - \frac{1}{2}T)$	$T \frac{\sin \frac{\omega T}{2}}{\frac{\omega T}{2}}$	

Fourier Transform of derivative:

Fourier transform of $\frac{dx(t)}{dt}$:

if $F(x(t)) \rightarrow X(\omega)$,

$$F\left(\frac{dx}{dt}\right) = \int_{-\infty}^{\infty} \frac{dx}{dt} e^{-j\omega t} dt$$

integrate by parts $\int u dv = uv - \int v du$
 $u = e^{-j\omega t}$
 $dv = \frac{dx}{dt} dt$, $v = x$, $du = -j\omega e^{-j\omega t} dt$





$$= \underbrace{x(t) e^{-j\omega t}}_{v \cdot u} \Big|_{t=-\infty}^{\infty} - \int_{-\infty}^{\infty} \underbrace{x(t) (-j\omega e^{j\omega t})}_{v du} dt$$

assuming
 $x(t) \rightarrow 0$
 $\omega t \rightarrow \pm\infty$

$$= 0 + j\omega \underbrace{\int_{-\infty}^{\infty} x(t) e^{-j\omega t} dt}_{X(\omega)}$$

$$= j\omega X(\omega)$$

A real Fourier transform

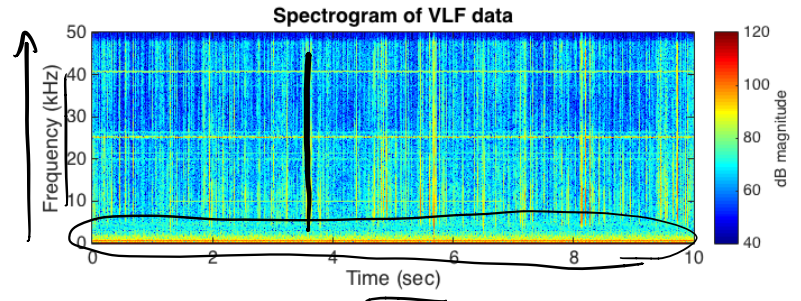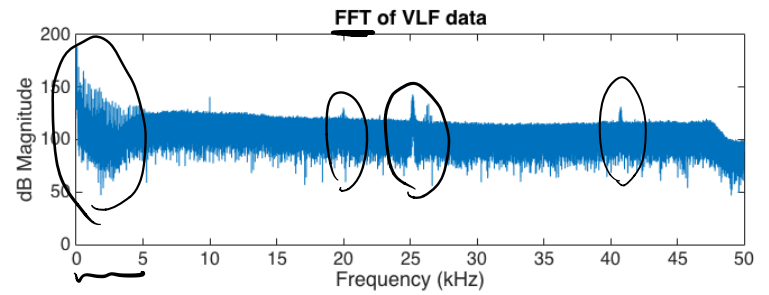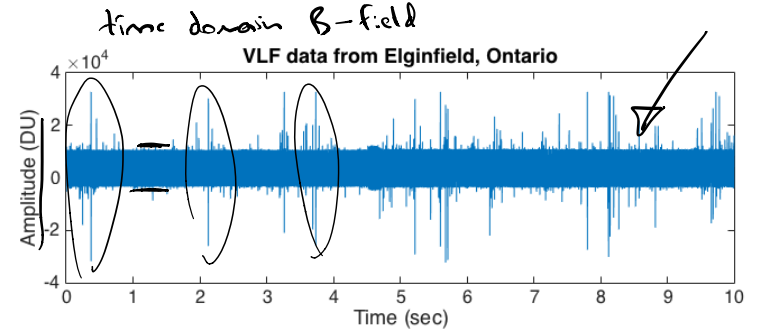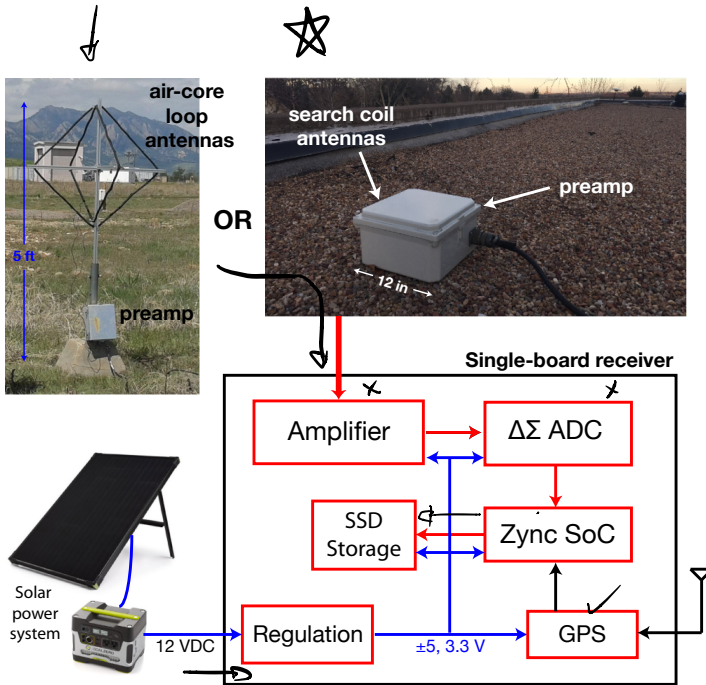

Comparing Fourier Series and Transform

FS: $x(t) = a_0 + \sum_{i=1}^{\infty} c_i e^{j\omega_i t} = a_0 + \sum_{i=1}^{\infty} (a_i \cos \omega_i t + b_i \sin \omega_i t)$

↑
volts

domain: discrete frequencies

units: volts

signal: must be periodic

FT: $x(\omega) = \int_{-\infty}^{\infty} x(t) e^{-j\omega t} dt \Rightarrow x(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} x(\omega) e^{j\omega t} d\omega$

domain: continuous in freq

units: V/Hz or V·s

signal: any

Comparing Laplace and Fourier Transform

LT: $X(s) = \int_{0^+}^{\infty} x(t) e^{-st} dt$

$$s = \sigma + j\omega$$

↑ ↑
 $\text{Re}\{s\}$ $\text{Im}\{s\}$

units
domain
signal } same

FT: $X(\omega) = \int_{-\infty}^{\infty} x(t) e^{-j\omega t} dt$



$$X(\omega) = \int_{-\infty}^{\infty} x(t) e^{-j\omega t} dt$$

DFT: $X_k = \sum_{n=0}^{N-1} x_n e^{-j2\pi kn/N}$

N = total number of samples

n = index in time of x

k = index in freq of X

FFT = Fast Fourier Transform

Complex Impedances

if my signal is $v(t) = V_0 e^{j\omega t}$, $i(t) = I_0 e^{j\omega t}$

Resistor:

$$v(t) = i(t) \cdot R$$

$$V(\omega) = I(\omega) \cdot R$$

$$\frac{V(\omega)}{I(\omega)} = Z_R(\omega) = R$$

Capacitor:

$$i(t) = C \frac{dv(t)}{dt}$$

$$I(\omega) = C \cdot j\omega V(\omega)$$

$$\frac{V(\omega)}{I(\omega)} = Z_C(\omega) = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$



Inductor:

$$v(t) = L \frac{di(t)}{dt}$$

$$V(\omega) = L \cdot j\omega I(\omega)$$


$$\frac{V(\omega)}{I(\omega)} = Z_L(\omega) = j\omega L$$

capacitor: current leads voltage by 90°

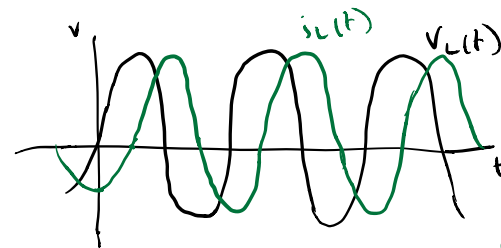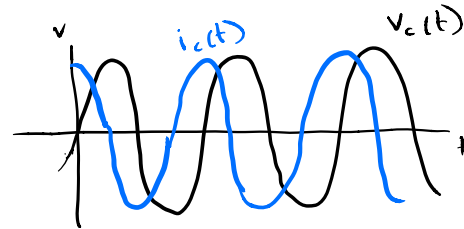


inductor: current lags voltage by 90°

Complex Impedances

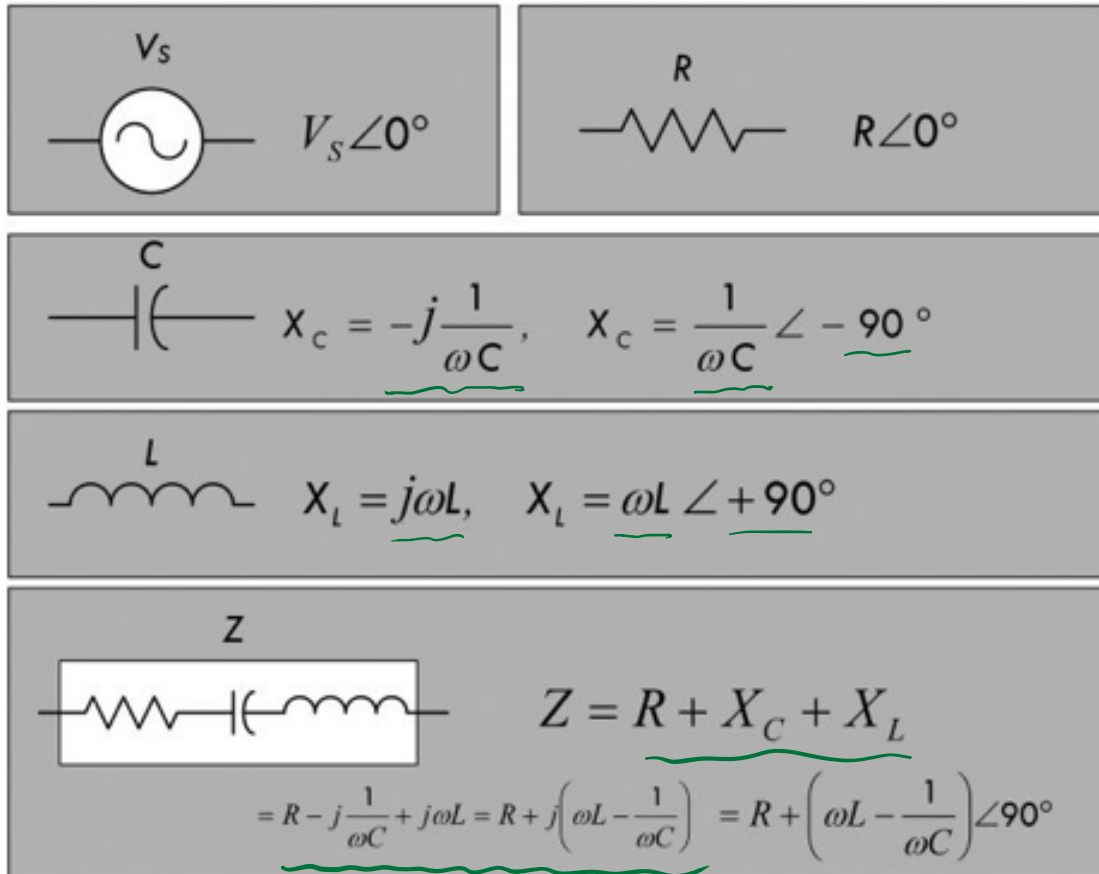


Complex Impedance Phase delay

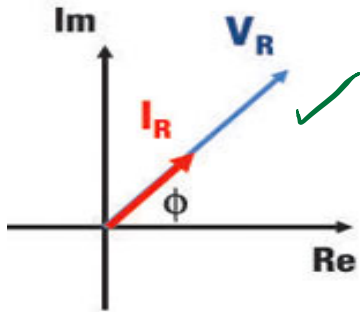


Resistor

Voltage in phase with current

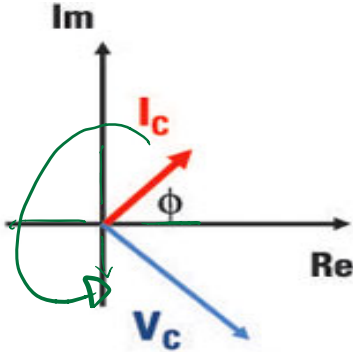

Capacitor

Voltage lags current by 90°

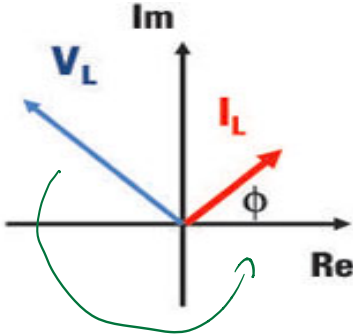


Inductor



Voltage leads current by 90°

Signal Conditioning (again)

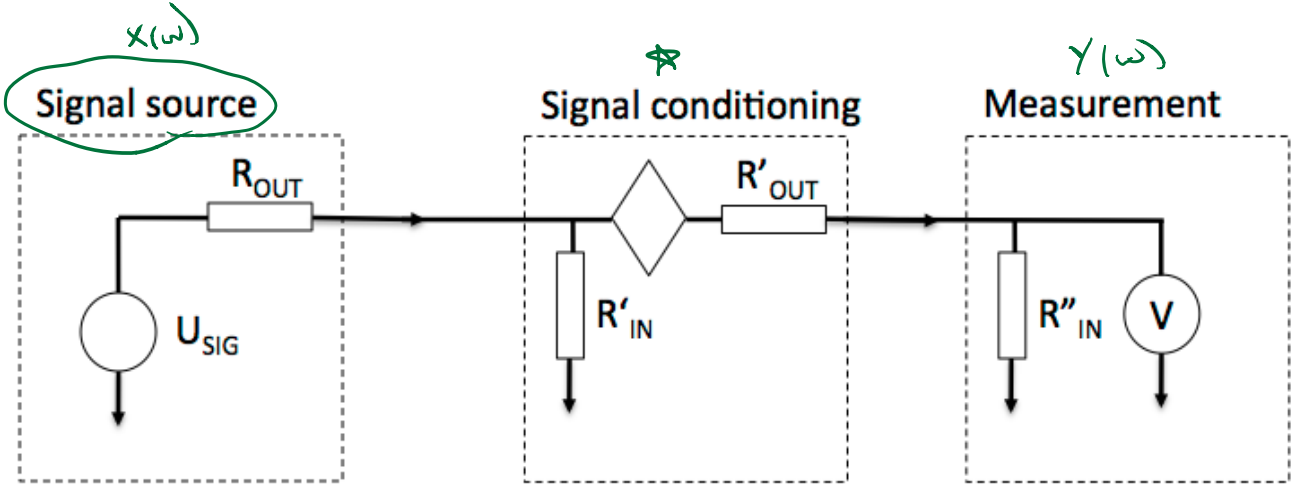- ❖ Level shifting
- ❖ Gain / attenuation
- ★ ❖ **Filtering**
- ❖ Buffering
- ❖ Impedance conversion



Voltage Divider

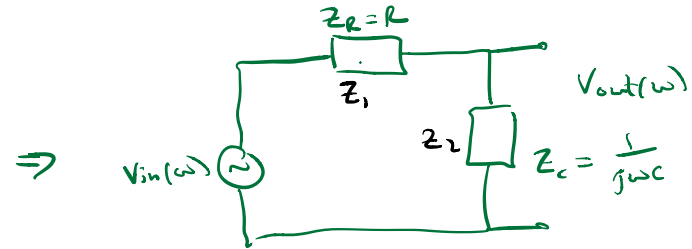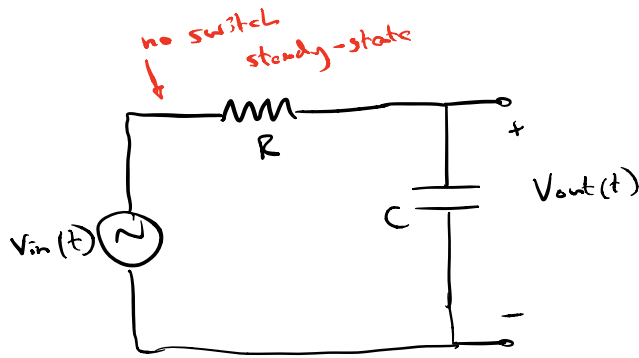

$$V_{out}(\omega) = V_{in}(\omega) \cdot \left[\frac{Z_2}{Z_1 + Z_2} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC} \right]$$

$$\frac{V_{out}(\omega)}{V_{in}(\omega)} = H(\omega) = \frac{1}{1 + j\omega RC} \quad \text{is the transfer function.$$


$$H(\omega) = |H(\omega)| e^{j\phi(\omega)}$$

$$|H(\omega)| = (H(\omega) \cdot H^*(\omega))^{1/2} \quad \text{magnitude response}$$

$$\phi(\omega) = \tan^{-1} \left(\frac{\text{Im}\{H(\omega)\}}{\text{Re}\{H(\omega)\}} \right) \quad \text{phase response}$$

Voltage Divider cont.

⇒ Magnitude Response.

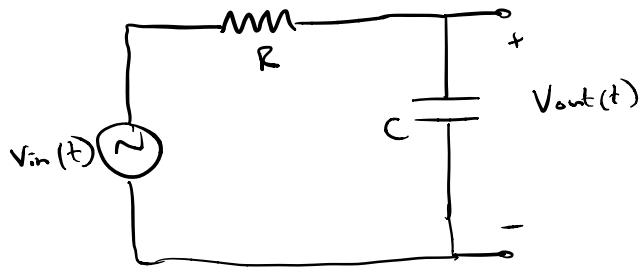

$$\left| \frac{V_{out}(\omega)}{V_{in}(\omega)} \right| = |H(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$\phi(\omega) = -\tan^{-1}(\omega RC)$$



$2\pi f$
↑

at $\omega = 0$, $|H(\omega)| = 1$


at $\omega \rightarrow \infty$, $|H(\omega)| = 0$

at $\omega_0 = 1/RC$, $|H(\omega)| = 1/\sqrt{2}$

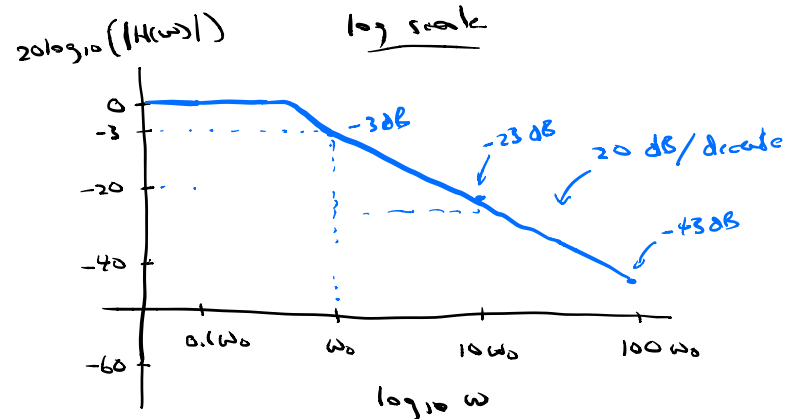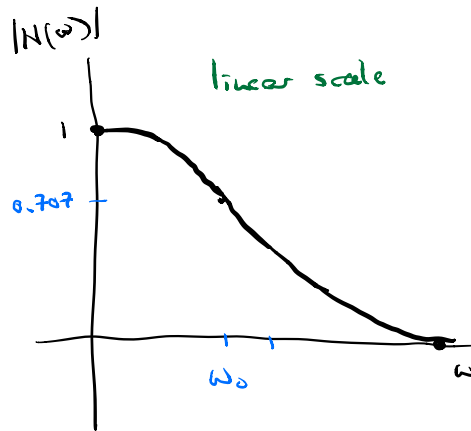$\omega_0 =$ cutoff freq. OR -3 dB frequency




Low-pass filter

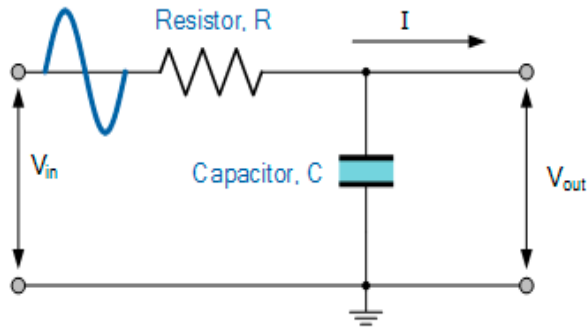


$$\frac{V_{out}}{V_{in}} = \frac{Z_C}{Z_R + Z_C} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC} = H(\omega)$$

★

$$\left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{1}{1 + j\omega RC} \right| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

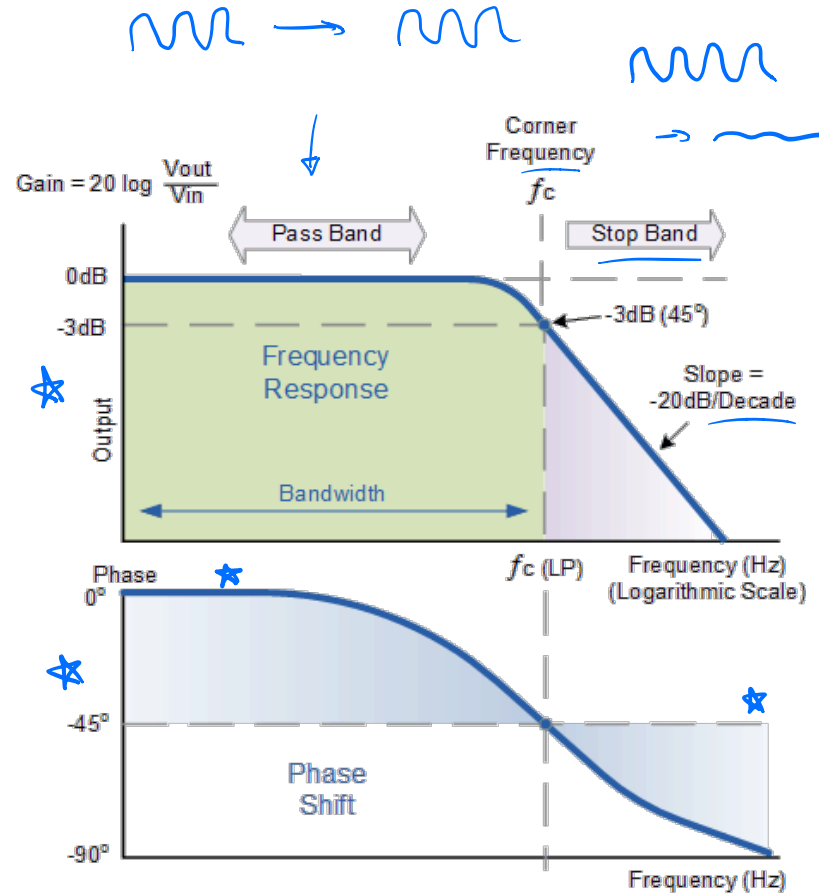

What about this one?

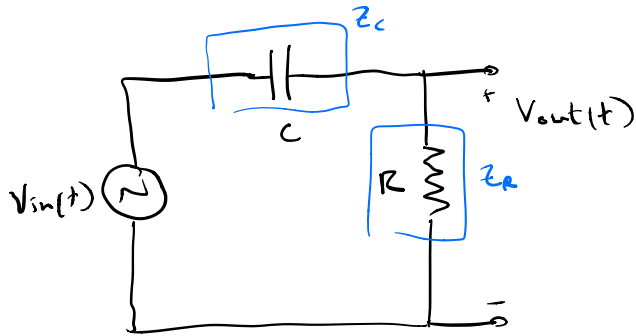

$$\frac{V_{out}(\omega)}{V_{in}(\omega)} = H(\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$

magnitude: $|H(\omega)| = \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}}$




$$\phi(\omega) = \tan^{-1}(\omega RC)$$

at $\omega = 0$: $|H(\omega)| = 0$


at $\omega \rightarrow \infty$: $|H(\omega)| = 1$

at $\omega = 1/RC$: $|H(\omega)| = 1/\sqrt{2}$

High-pass filter cont.

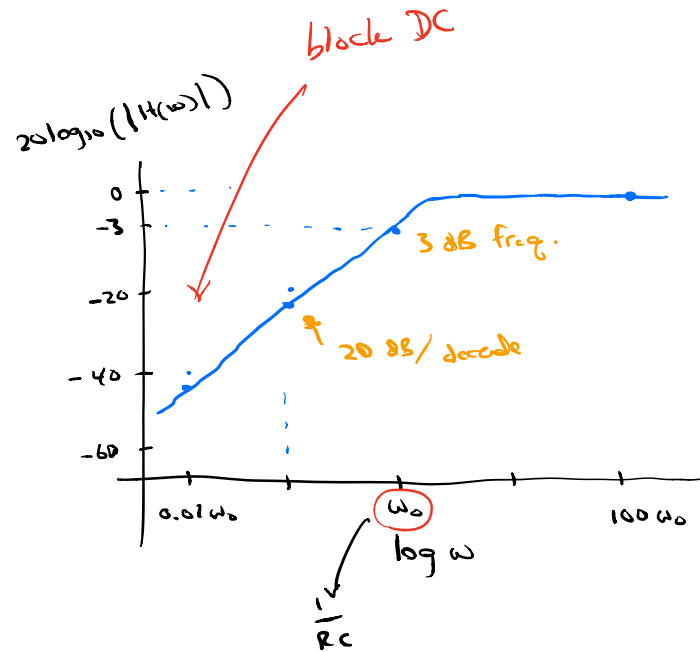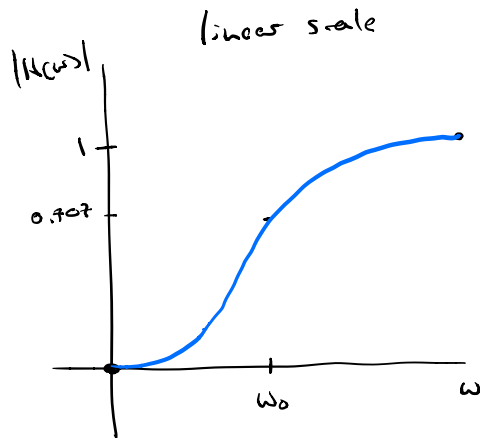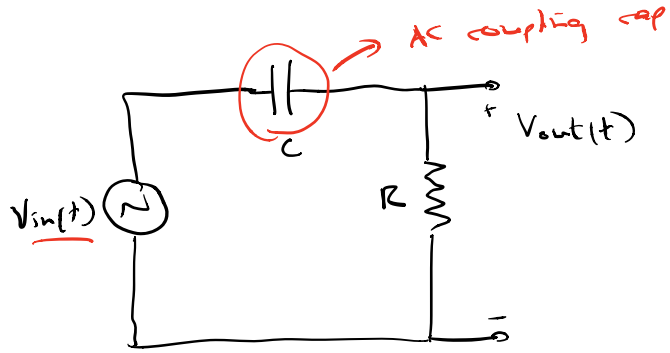


High-pass filter

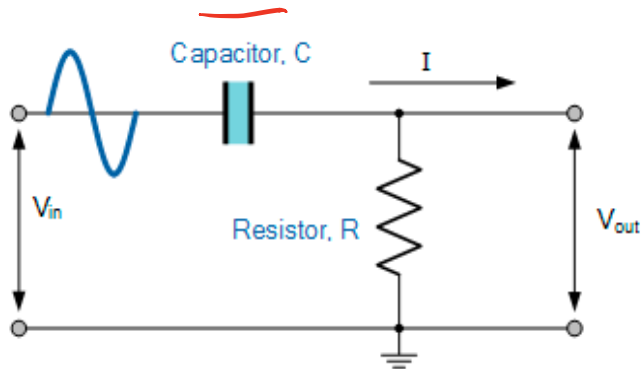


$$\frac{V_{OUT}}{V_{IN}} = H(\omega) = \frac{j\omega RC}{1 + j\omega RC}$$

$$\left| \frac{V_{OUT}}{V_{IN}} \right| = \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}}$$

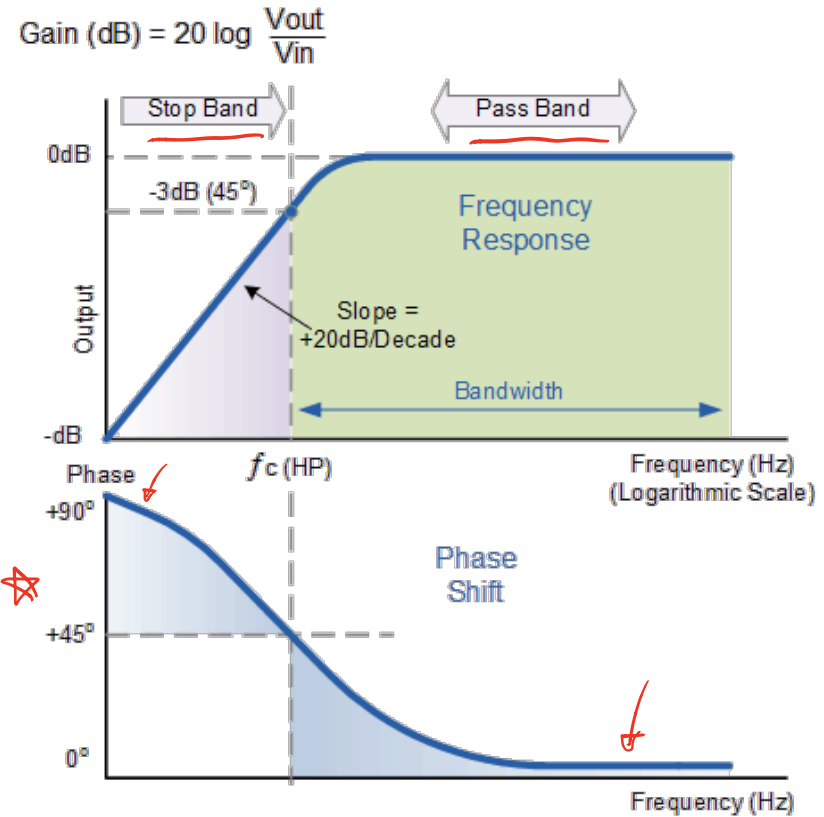

What about this one??

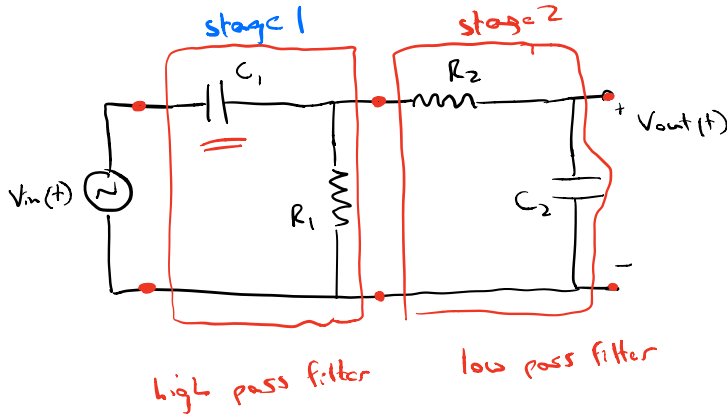

$$|H(\omega)| = |H_1(\omega)| \cdot |H_2(\omega)|$$

$$|H(\omega)| = \frac{\omega R_1 C_1}{\sqrt{1 + \omega^2 R_1^2 C_1^2}} \cdot \frac{1}{\sqrt{1 + \omega^2 R_2^2 C_2^2}}$$


at $\omega = 0$: $|H(\omega)| = 0$

at $\omega = \infty$: $|H(\omega)| = 0$

at $\omega_{01} = 1/R_1 C_1$: $|H(\omega)| = 1/\sqrt{2}$
 at $\omega_{02} = 1/R_2 C_2$: $|H(\omega)| = 1/\sqrt{2}$

} if R, C chosen carefully

$20 \log_{10}(|H(\omega)|)$

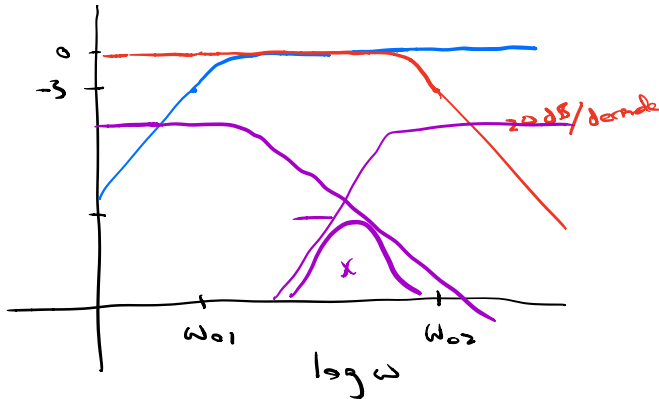

same

